

CS184a: Computer Architecture (Structures and Organization)

Day8: October 18, 2000
Computing Elements 1:
LUTs

Last Time


- Instruction Space Modeling
 - huge range of densities
 - huge range of efficiencies
 - large architecture space
 - modeling to understand design space
- Started on Empirical Comparisons
 - [not sure when we'll finish this up]

Today

- Look at Programmable Compute Blocks
- Specifically LUTs Today
- Recurring theme:
 - define parameterized space
 - identify costs and benefits
 - look at typical application requirements
 - compose results, try to find best point


Compute Function

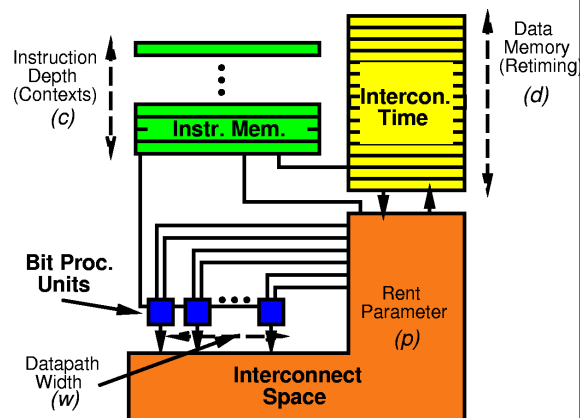- What do we use for “compute” function
- Any Universal
 - NANDx
 - ALU
 - LUT




Lookup Table

 - Load bits into table
 - 2^N bits to describe
 - $\Rightarrow 2^{2^N}$ different functions
- Table translation
 - performs logic transform



Lookup Table


 


We could...


- Just build a large memory = large LUT
- Put our function in there
- What's wrong with that?

FPGA = Many small LUTs

Alternative to one big
LUT

  

Toronto FPGA Model

 

Caltech CS184a Fall2000

9

What's best to use?

- Small LUTs
- Large Memories
- ...small LUTs or large LUTs
- ...or, how big should our memory blocks used to perform computation be?


Caltech CS184a Fall2000 -- DeHon

10

Start to Sort Out: Big vs. Small Luts

- Establish equivalence
 - how many small LUTs equal one big LUT?

“gates” in 2-LUT ?

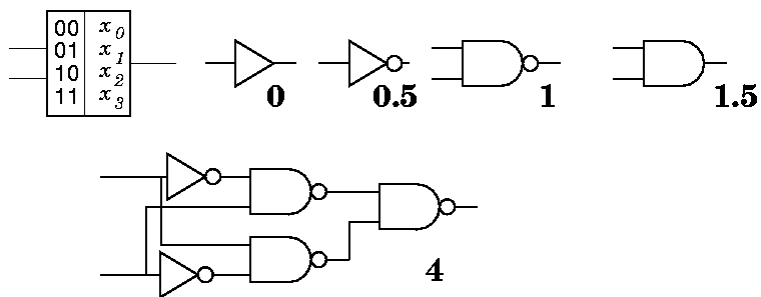

How Much Logic in a LUT?


- Lower Bound?
 - Concrete: 4-LUTs to implement M-LUT
- Not use all inputs?
 - 0 ... maybe 1
- Use all inputs?
 - $(M-1)/3$
 - example M-input AND
 - cover 4 ins w/ first 4-LUT,
 - 3 more and cascade input with each additional
 - $(M-1)/k$ for K-lut

Caltech CS184a Fall2000 -- DeHon

13

How much logic in a LUT?

 - Upper Upper Bound:
 - M-LUT implemented w/ 4-LUTs
 - $M\text{-LUT} \leq 2^{M-4} + (2^{M-4} - 1) \leq 2^{M-3}$ 4-LUTs



Caltech CS184a Fall2000 -- DeHon

14

How Much?

- Lower Upper Bound:
 - 2^{2^M} functions realizable by M-LUT
 - Say Need n 4-LUTs to cover; compute n :
 - strategy count functions realizable by each
 - $(2^{2^4})^n \geq 2^{2^M}$
 - $n \log(2^{2^4}) \geq \log(2^{2^M})$
 - $n 2^4 \log(2) \geq 2^M \log(2)$
 - $n 2^4 \geq 2^M$
 - $n \geq 2^{M-4}$

How Much?

- Combine
 - Lower Upper Bound
 - Upper Lower Bound
 - (number of 4-LUTs in M-LUT)

$$2^{M-4} \leq n \leq 2^{M-3}$$

Memories and 4-LUTs

- For the **most complex** functions an M-LUT has $\sim 2^{M-4}$ 4-LUTs
- SRAM 32Kx8 $\lambda=0.6\mu\text{m}$
 - $170\text{M}\lambda^2$ (21ns latency)
 - $8 \cdot 2^{11} = 16\text{K}$ 4-LUTs
- XC3042 $\lambda=0.6\mu\text{m}$
 - $180\text{M}\lambda^2$ (13ns delay per CLB)
 - 288 4-LUTs
- Memory is 50+x denser than FPGA

Caltech CS184a Fall2000 -- DeHon
– ...and faster

17

Memory and 4-LUTs


- For “regular” functions?
- 15-bit parity
 - entire 32Kx8 SRAM
 - 5 4-LUTs
 - (2% of XC3042 $\sim 3.2\text{M}\lambda^2 \sim 1/50\text{th}$ Memory)
- 7b Add
 - entire 32Kx8 SRAM
 - 14 4-LUTs
 - (5% of XC3042, $8.8\text{M}\lambda^2 \sim 1/20\text{th}$ Memory)

Caltech CS184a Fall2000 -- DeHon

18

LUT + Interconnect

 
- Interconnect allows us to exploit **structure** in computation
- Already know
 - LUT Area \ll Interconnect Area
 - Area of an M-LUT on FPGA \gg M-LUT Area
- ...but most M-input functions
 - complexity $\ll 2^M$



Different Instance, Same Concept

- Most general functions are huge
- Applications exhibit structure
- Exploit structure to optimize “common” case

LUT Count vs. base LUT size

 


Caltech CS184a Fall2000 -- DeHon

21

LUT vs. K

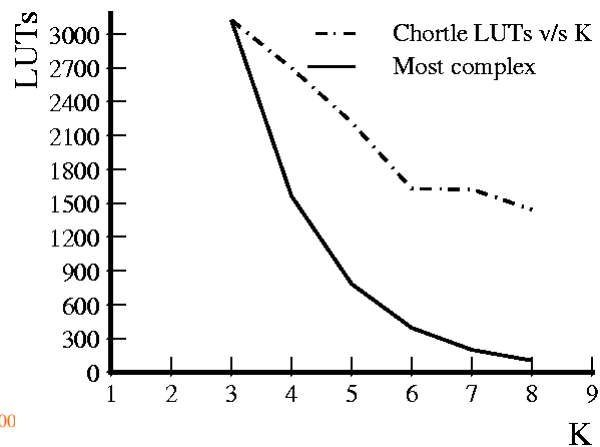- DES MCNC Benchmark
 - moderately irregular



Caltech CS184a Fall2000

22

Toronto Experiments


- Want to determine best K for LUTs
- Bigger LUTs
 - handle complicated functions efficiently
 - less interconnect overhead
- Smaller LUTs
 - handle regular functions efficiently
 - interconnect allows exploitation of compute structure
- What's the typical complexity/structure?

Familiar Systematization

- Define a design/optimization space
 - pick key parameters
 - e.g. K = number of LUT inputs
- Build a cost model
- Map designs \mathcal{D} look at resource costs at each point
- Compose: Logical Resources $\hat{\quad}$ Resource Cost
- Look for best design points


Toronto LUT Size

 - Map to K-LUT
 - use Chortle
- Route to determine wiring tracks
 - global route
 - different channel width W for each benchmark
- Area Model for K and W





LUT Area vs. K

- Routing Area roughly linear in K

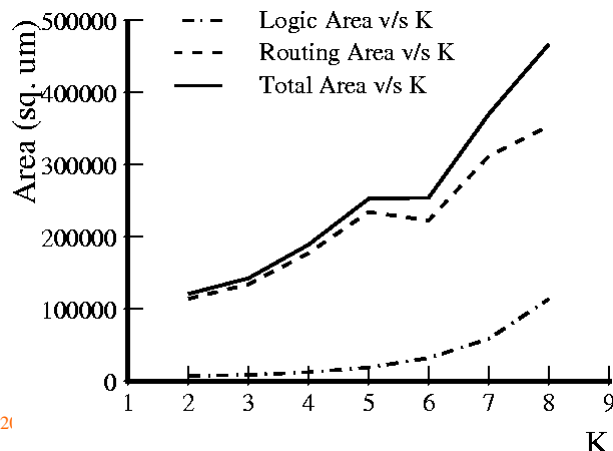

Mapped LUT Area


- Compose Mapped LUTs and Area Model

  

Caltech CS184a Fall2000 -- DeHon

27

Mapped Area vs. LUT K

 

N.B. unusual case minimum area at K=3


Caltech CS184a Fall2000 -- DeHon

28

Toronto Result

- Minimum LUT Area
 - at $K=4$
 - Important to note minimum on previous slides based on particular cost model
 - robust for different switch sizes
 - (wire widths)
 - [see graphs in paper]

Implications

 

Implications

- Custom? / Gate Arrays?
- More restricted logic functions?

Relate to Sequential?

- How does this result relate to sequential execution case?
- Number of LUTs = Number of Cycles
- Interconnect Cost?
 - Naïve
 - structure in practice?
- Instruction Cost?

Delay


Back to Spatial
(save for day10)...

Delay?

- Circuit Depth in LUTs?
- “Simple Function” --> M-input AND
 - 1 table lookup in M-LUT
 - $\log_k(M)$ in K-LUT

Delay?

 - M-input “Complex” function
 - 1 table lookup for M-LUT
 - between: $\lceil (M-K)/\log_2(k) \rceil + 1$
 - and $\lceil (M-K)/\log_2(k - \log_2(k)) \rceil + 1$




Delay

- Simple: $\log M$
- Complex: linear in M

- Both go as $1/\log(k)$

Circuit Depth vs. K

 


Caltech CS184a Fall2000 -- DeHon

37

LUT Delay vs. K

 
- For small LUTs:
 - $t_{LUT} \approx c_0 + c_1 \times K$
- Large LUTs:
 - add length term
 - $c_2 \times \sqrt{2^K}$
- Plus Wire Delay
 - $\sim \sqrt{\text{area}}$



Caltech CS184a Fall2000 -- DeHon

38

Delay vs. K

 

Why not
satisfied
with this
model?

$$\text{Delay} = \text{Depth} \times (t_{\text{LUT}} + t_{\text{Interconnect}})$$

Caltech CS184a Fall2000 -- DeHon

39

Observation

- General interconnect is expensive
- “Larger” logic blocks
 - => less interconnect crossing
 - => lower interconnect delay
 - => get larger
 - => get slower
 - faster than modeled here due to area
 - => less area efficient
 - don't match structure in computation

Caltech CS184a Fall2000 -- DeHon

40

Finishing Up...

No Class Monday

CS Dept. Retreat Sun/Mon.
André **not** read email on Sunday.
Catchup on reading, assignment,
sleep...
see you Wednesday.

Big Ideas

[MSB Ideas]

- Memory most dense programmable structure for the **most complex** functions
- Memory inefficient (scales poorly) for structured compute tasks
- Most tasks have some structure
- Programmable Interconnect allows us to exploit that structure

Big Ideas

[MSB-1 Ideas]

- Area
 - LUT count decrease w/ K , but slower than exponential
 - LUT size increase w/ K
 - exponential LUT function
 - empirically linear routing area
 - Minimum area around $K=4$

Big Ideas

[MSB-1 Ideas]

- Delay
 - LUT depth decreases with K
 - in practice closer to $\log(K)$
 - Delay increases with K
 - small K linear + large fixed term
 - minimum around 5-6